Stop ‘n’ Search

TAG3

Typical connections for TAG III to a door with access control.

The door is held locked via the TAGIII relay 2 clean contact. The access controller acts as an input to the TAGIII. When the input is seen, the TAGIII randomly selects for searching or allows to pass. If you are allowed to pass, the green led will illuminate and relay 2 will switch to unlock the door and allow you to pass, when you open and close the door the unit will be ready for the next input. If you are selected to be searched, the unit will indicate so and relay 2 will not switch, therefore leaving the door locked.

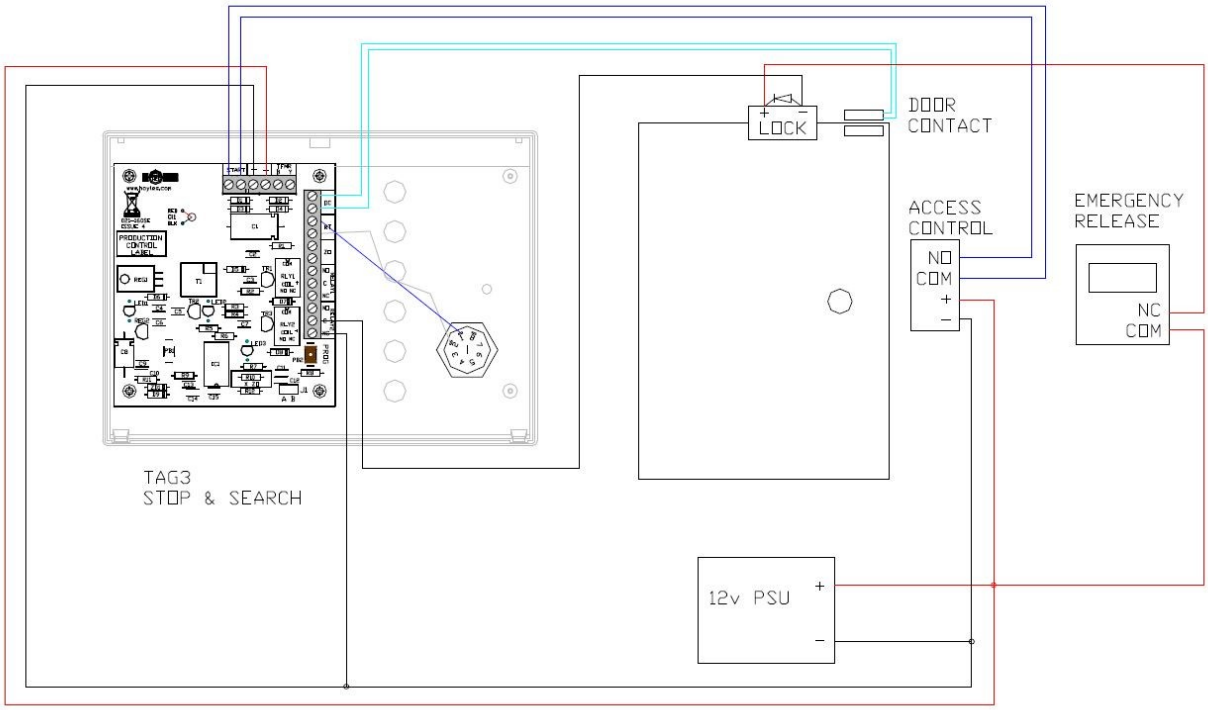

Hoyles Electronic Developments Ltd
Sandwash Close, Rainford, St Helens, WA11 8LY, UK
www.hoyles.com
sales@hoyles.com
+ 44 (0) 1744 886600